 


# ALU DESIGN

## Question:

Design a simple ALU for the following functions using Mux. Create the symbols and simulate the ALU, also find out the Propagation delay for each function.



| S1 | S0 | Function     |
|----|----|--------------|
| 0  | 0  | $A+B$        |
| 0  | 1  | $\sim A$     |
| 1  | 0  | $A \wedge B$ |
| 1  | 1  | $AB$         |


Here we need to create a 4 x 1 multiplexer. This takes four inputs and based on the values of selection lines gives one output.

Consider the inputs to be  $I_0$ ,  $I_1$ ,  $I_2$  and  $I_3$ , the select lines be  $S_0$  and  $S_1$ , then the output will be:


$$Y = S_1'S_0'I_0 + S_1'S_0I_1 + S_1S_0'I_2 + S_1S_0I_3$$

We implement this in Cadence using four 3-input AND gates and 2 2-input OR gate in CMOS logic with sizing ratio of 3:1.


Now the **MUX** schematic will be:

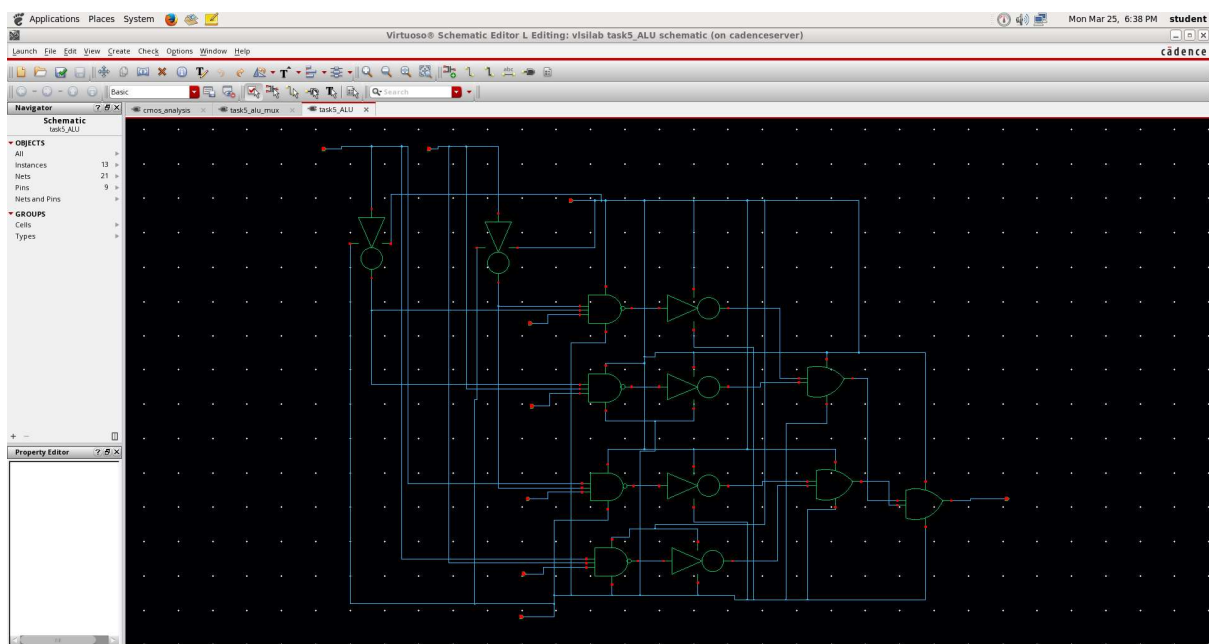

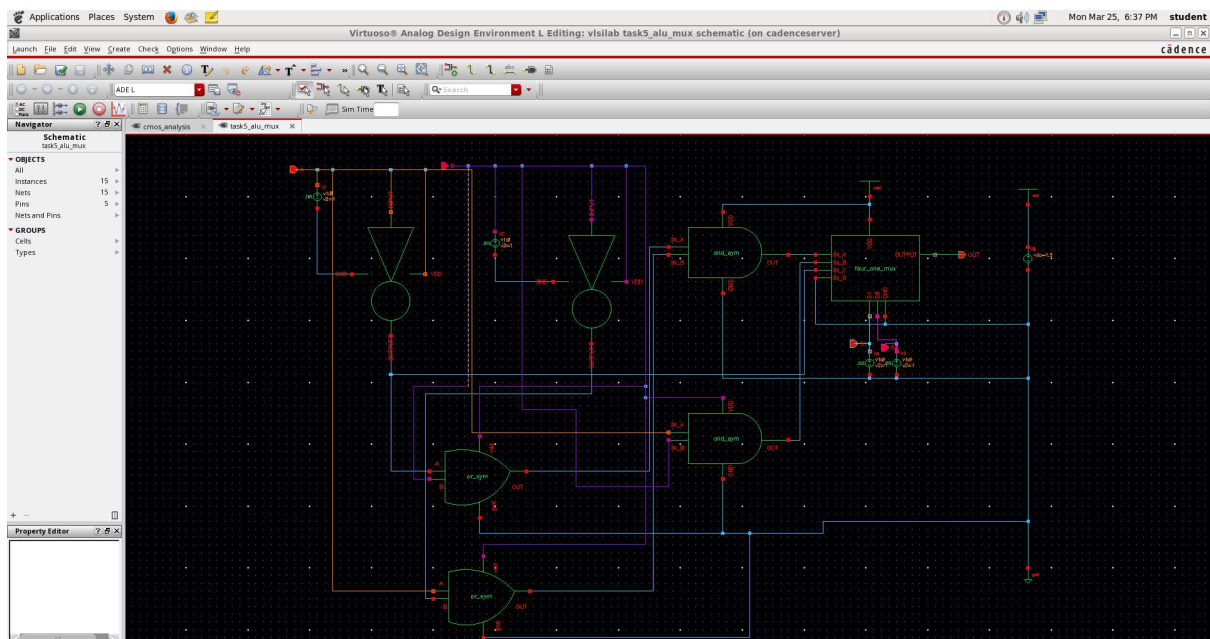Now the complete circuit to Implement the ALU is:



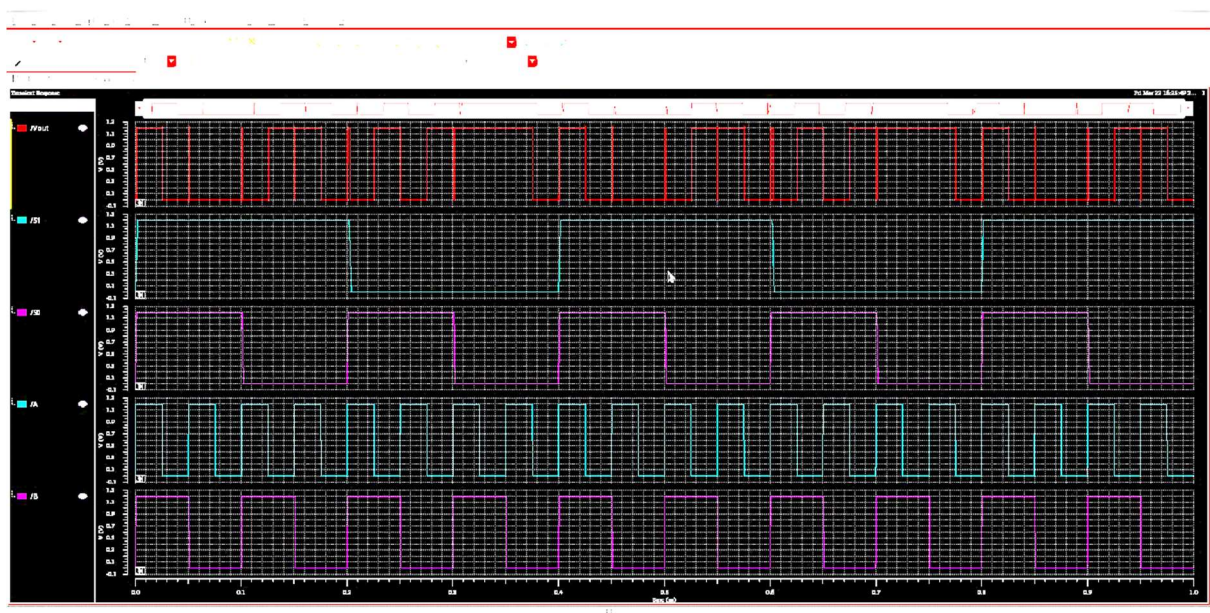On running this circuit, we observe the following output:



The output truth table is:

| <b>S1</b> | <b>S0</b> | <b>Function</b>                |
|-----------|-----------|--------------------------------|
| 0         | 0         | <b>A+B</b>                     |
| 0         | 1         | <b><math>\sim A</math></b>     |
| 1         | 0         | <b><math>A \wedge B</math></b> |
| 1         | 1         | <b>AB</b>                      |

This is the required output.